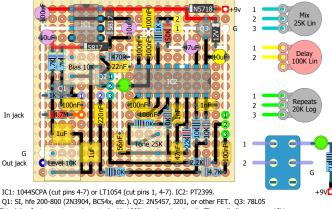
## The Hamlet Delay (The Procrastinator): Preamp and Delay with Tails

Circuit hacked together by Jon Patton. (cc) Creative commons, share alike, no money makin'.




This delay features a true mix control with 100% analog signal path. The audio line runs on 18V.

The tone trim goes from bright (sometimes noisy) to somewhat darker than the dry signal. I prefer ~33%. The footswitch is wired for tails, and thus the pedal is also an always-on, but transparent, preamp.

The volume pot can also be wired externally to use the pedal as a booster when the delay is off. Parts/values in red are optional. See schematic and/or build doc for notes and optional mods.

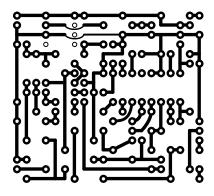A log pot for the Repeats is critical. Use the closest value you can get, as long as it's an A taper.



(cc) This circuit art is creative commons, share alike.